

EXPERIMENT-9

AIM: To design a 4-bit combinational shifter / logic shifter.

PLATFORM USED: Circuit verse

THEORY:


Shift micro-operations are used for the serial transfer of data and also support in conjunction with arithmetic, logic, and several data-processing operations. The contents of a register can be shifted to the left or the right. Information transferred through the serial input determines the type of shift.

There are three types of shift operation:


- Logical shift
- Circular shift
- Arithmetic shift

Symbolic Designation	Description
$R \leftarrow R1 \text{ shl } R$	Shift-left register R
$R \leftarrow R1 \text{ shr } R$	Shift-right register R
$R \leftarrow R1 \text{ cil } R$	Circular shift-left register R
$R \leftarrow R1 \text{ cir } R$	Circular shift-right register R
$R \leftarrow R1 \text{ ashl } R$	Arithmetic shift-left R
$R \leftarrow R1 \text{ ashr } R$	Arithmetic shift-right R

Symbolic representation

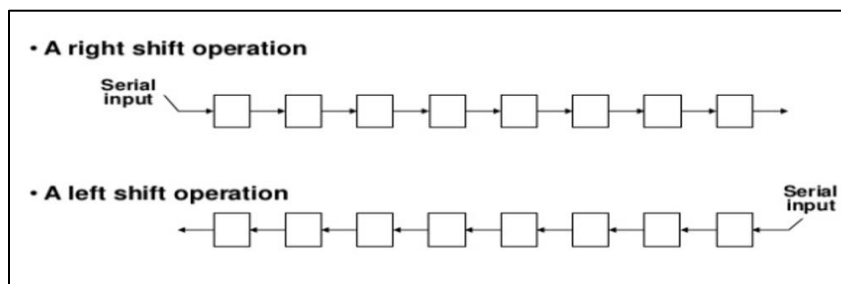

4-bit combinational circuit shifter

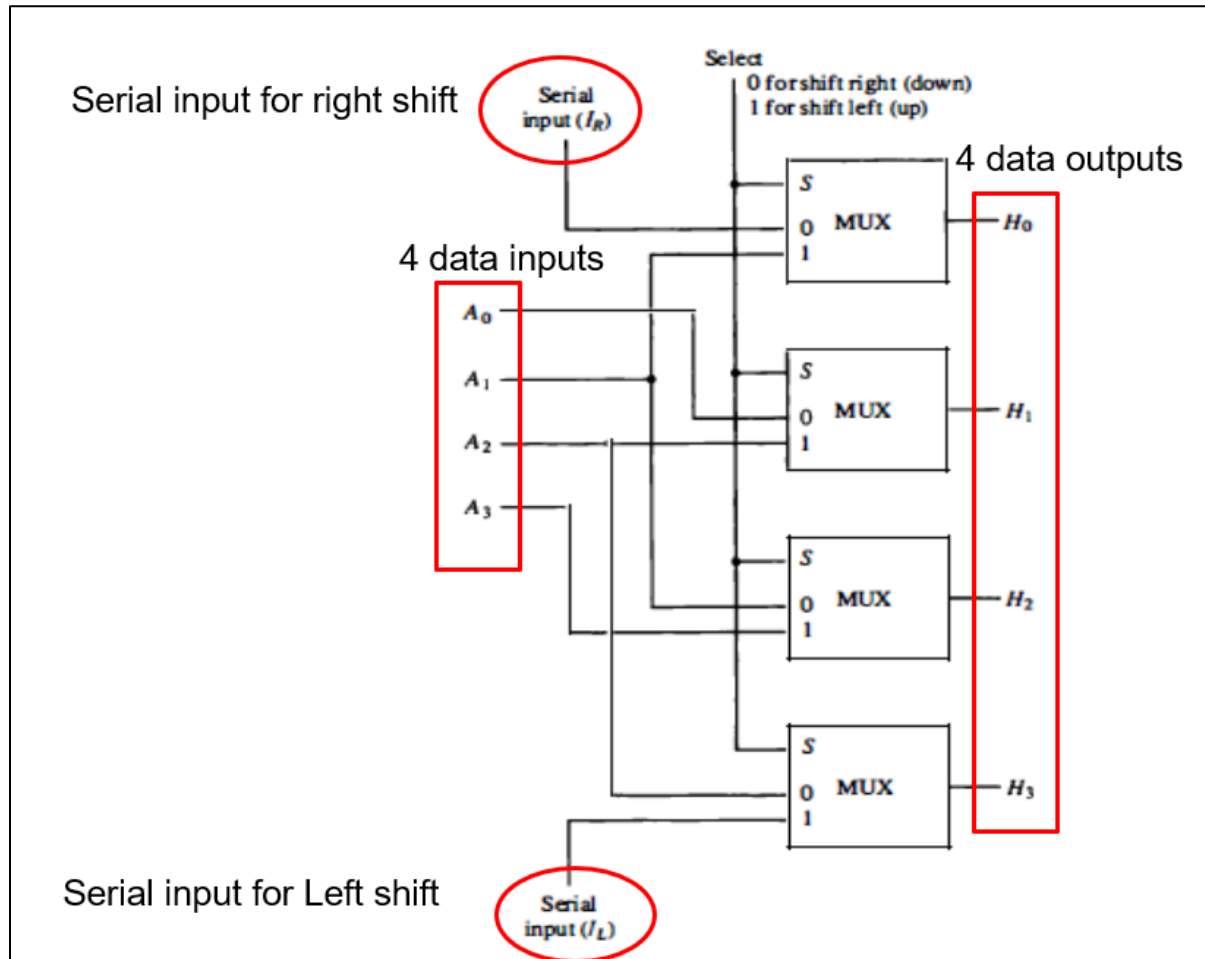


Truth table

Function table				
Select	Output			
S	H_0	H_1	H_2	H_3
0	I_R	A_0	A_1	A_2
1	A_1	A_2	A_3	I_L


When the selection input $S = 0$, the input data are shifted right (down in the diagram). When $S = 1$, the input data are shifted left (up in the diagram).

OUTPUT



LOGICAL RIGHT SHIFT

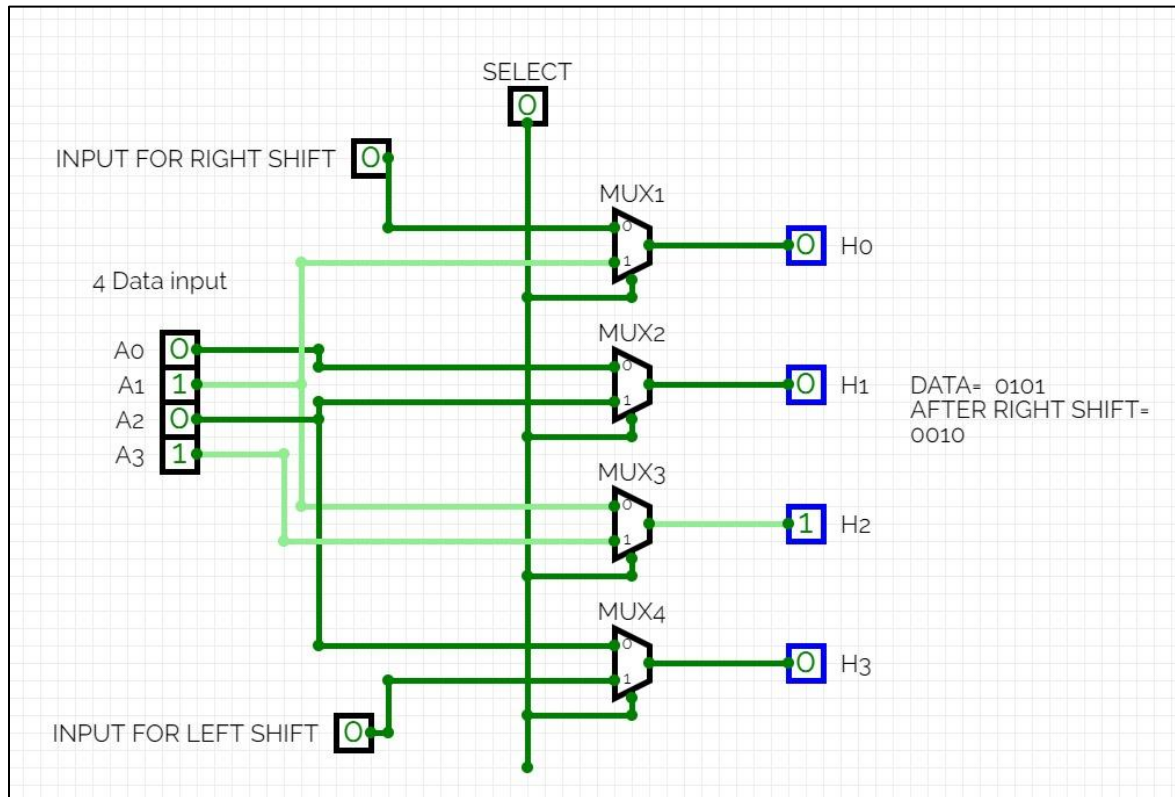

LOGICAL LEFT SHIFT

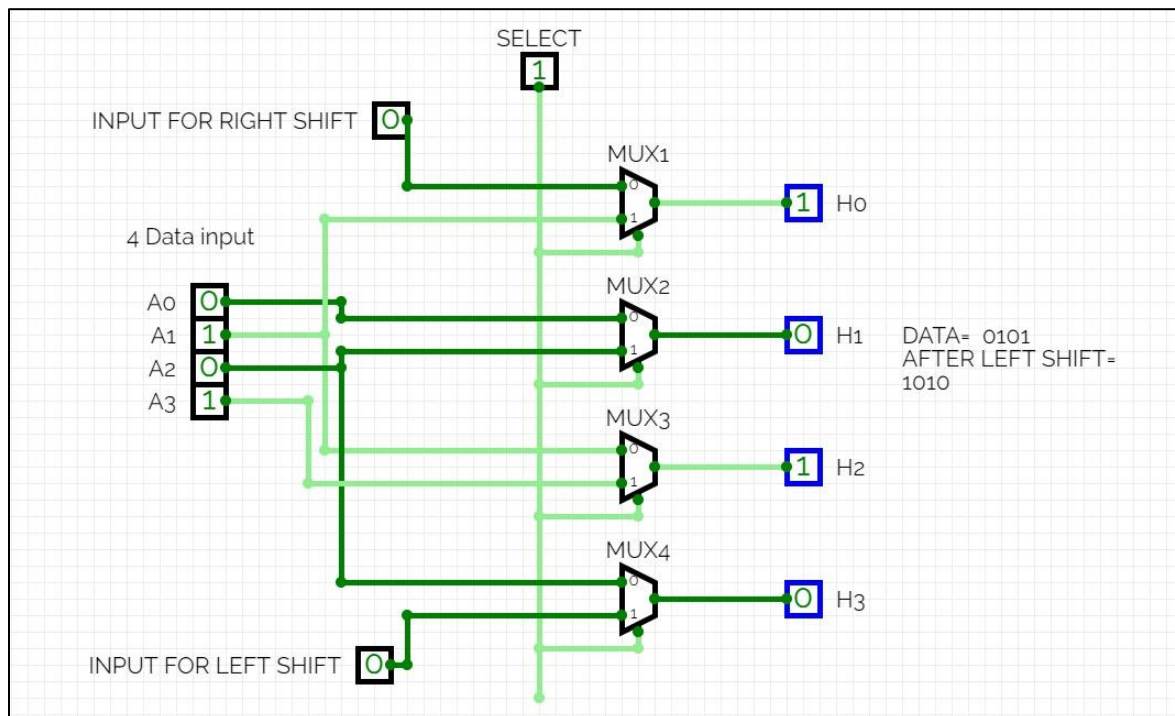

TIMING DIAGRAM

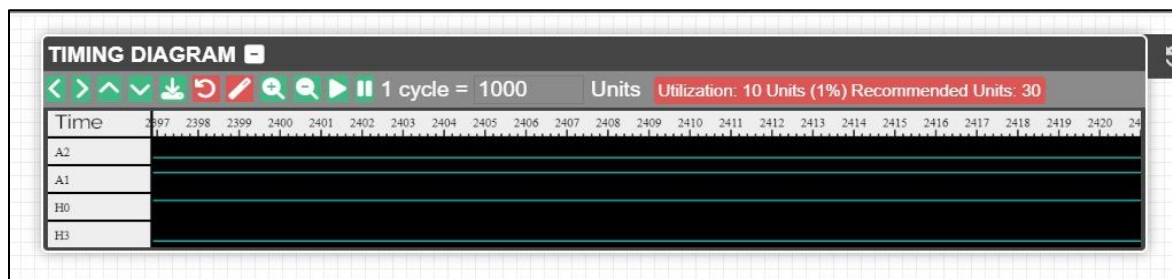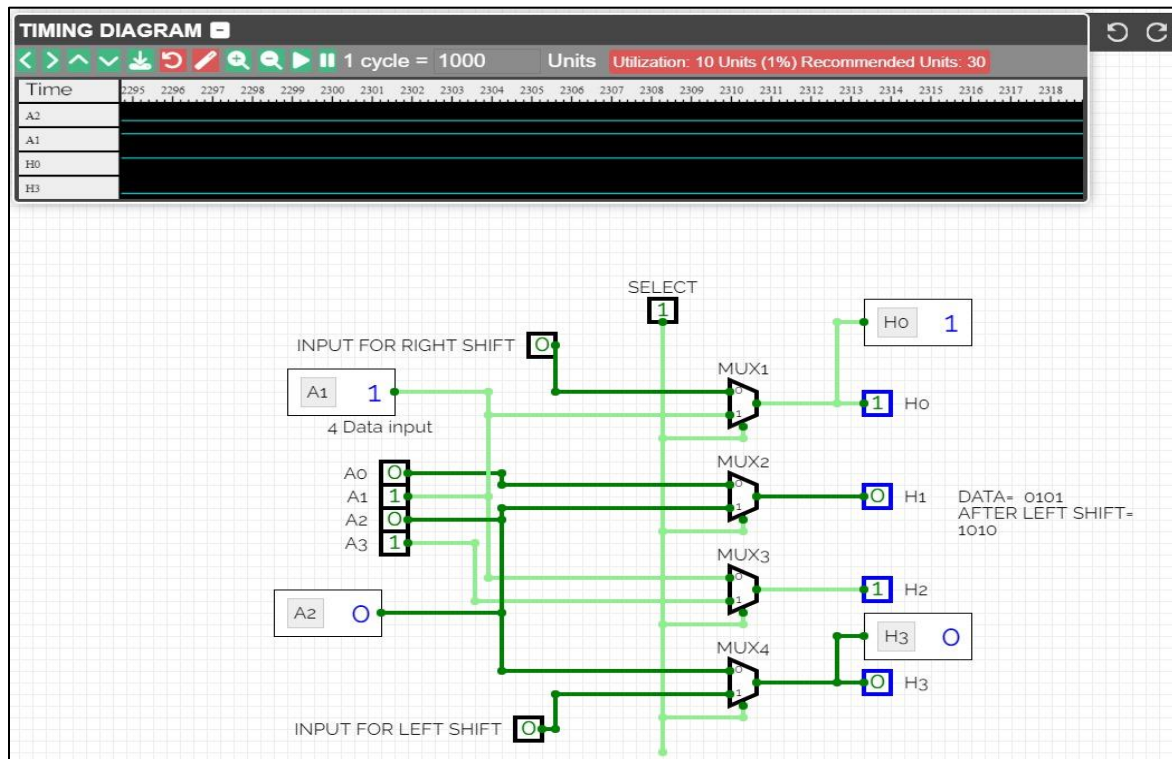

RESULT

4-bit combinational shifter has been designed successfully.

Criteria	Total Marks	Marks Obtained	Comments
Concept (A)	2		
Implementation (B)	2		
Performance (C)	2		
Total	6		